

FIGURE 4.24 The simple control and datapath are extended to handle the jump instruction. An additional multiplexor (at the upper right) is used to choose between the jump target and either the branch target or the expential instruction following this one. This multiplexor is controlled by the jump control signal. The jump target address is obtained by shifting the lower 26 bits of the jump instruction left 2 bits of bother) adding these lower the bits and then concatenating the upper 4 bits of PC+ 4 as the high-order bits, thus yielding a 22-bit address Capright © 2020 Bits of its Allrights reserved.