

# CIS 351 Sample ADD4 Problem Solutions

Mon 31<sup>st</sup> Jan, 2022

## ADD4: Recognize Overflow

Given an 4-bit adder, complete the table below to show the carry out and overflow for each pair of inputs.

A		B		$C_{out}$	Overflow
0	(0000)	0	(0000)	0	0
-1	(1111)	-1	(1111)	1	0
5	(0101)	6	(0110)	0	1