

Name: _____

CIS 351 Sample CL4 Problem

1 September 2025

CL4: Propagation Delay

Compute the propagation delay of the circuit below given the individual gate delays:

