CIS 351 Sample CL4 Problem Solutions

Tue $2^{\rm nd}$ Sept, 2025

CL4: Propagation Delay

Compute the propagation delay of the circuit below given the individual gate delays:

