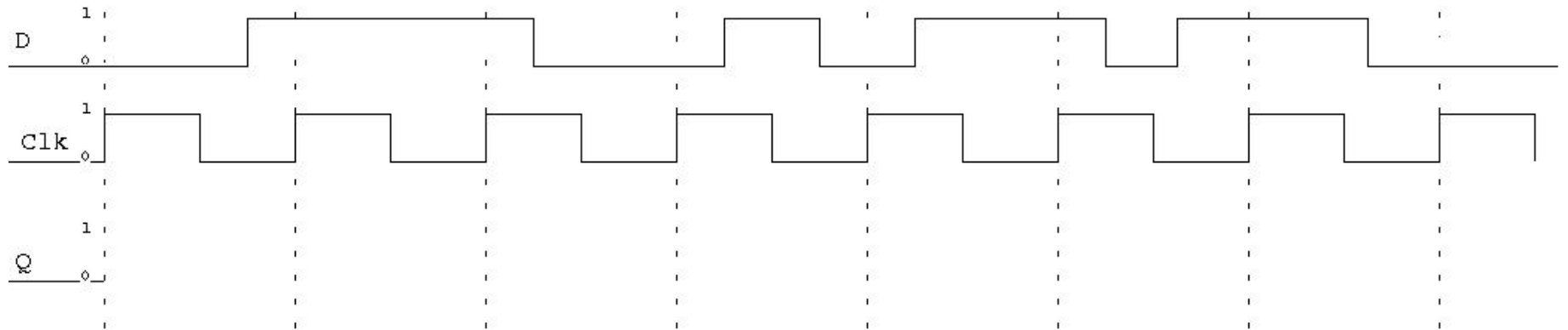


Name: \_\_\_\_\_

## Flip-Flop Quiz

Complete the timing diagram below to show the operation of a *rising-edge* flip-flop.



(Here is an extra copy, in case you made a mistake.)

