

Name: _____

CIS 351 Sample CL1 Problem

01 September 2025

CL1: Truth Tables

Construct a truth table that shows the output of a circuit that takes a four-bit integer as input and returns **true** if the input is a multiple of 5.

A	B	C	D	
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

CIS 351 Sample CL1 Problem Solutions

Mon 21st Sept, 2026

CL1: Truth Tables

Construct a truth table that shows the output of a circuit that takes a four-bit integer as input and returns **true** if the input is a multiple of 5.

A	B	C	D	
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1