

Name: _____

CIS 351 Sample CL4 Problem

1 September 2026

CL4: Draw Circuits

(a) Draw a circuit that implements the truth table below:

A	B	C	Out
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

(b) Draw a combinatorial circuit that implements this Boolean expression: $\overline{(AC)} + (B \oplus \bar{C})$


CIS 351 Sample CL4 Problem Solutions

Thu 24th Sept, 2026

CL4: Draw Circuits

(a) Draw a circuit that implements the truth table below:

A	B	C	Out
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

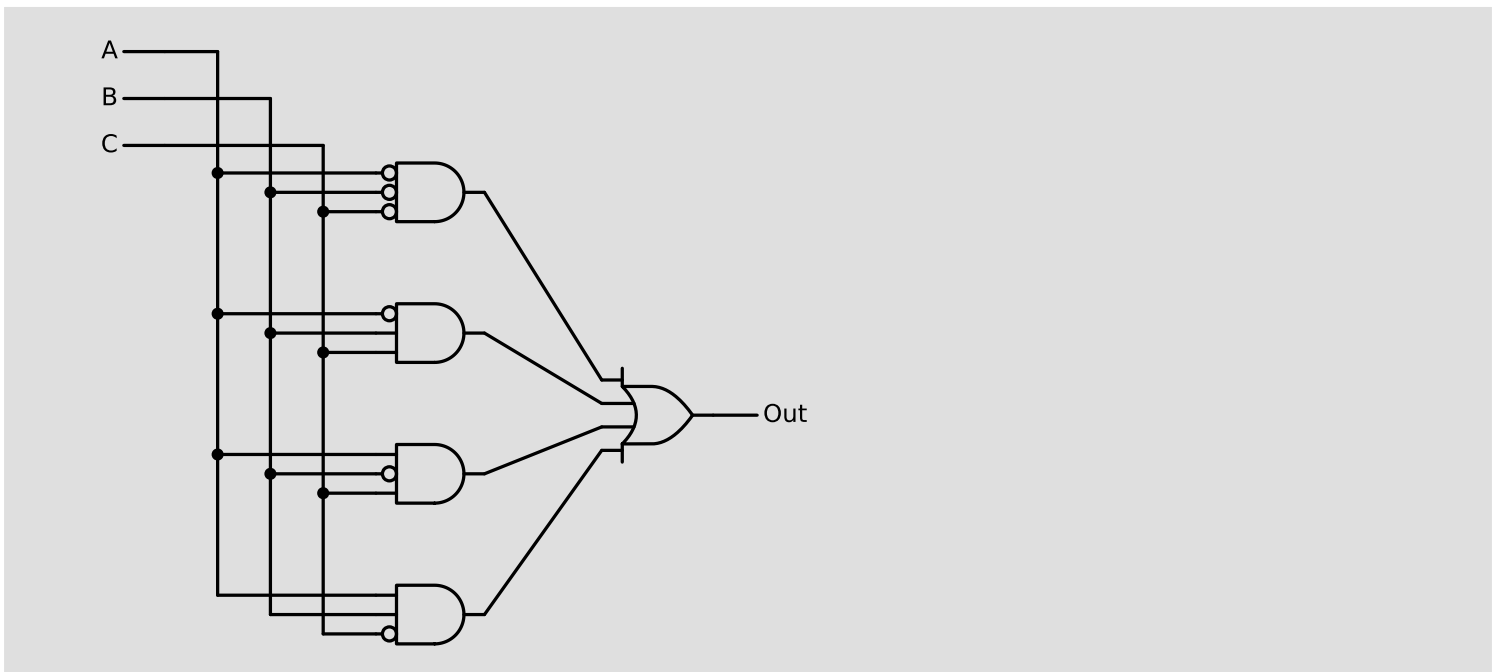

(b) Draw a combinatorial circuit that implements this Boolean expression: $\overline{AC} + (B \oplus \bar{C})$

