


Name: _____

CIS 351 Sample CL5 Problem

1 September 2026

CL5: Propagation Delay

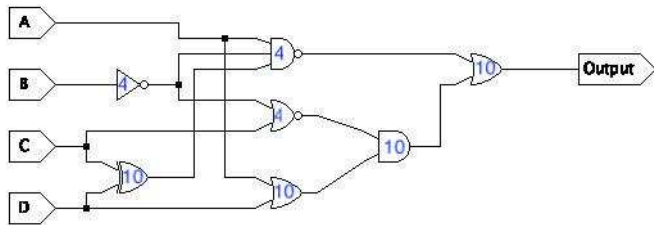Compute the propagation delay of the circuit below given the individual gate delays:



Circuit: $\overline{A\bar{B}(C \oplus D)} + \overline{(\bar{B} + C)}(A + D)$

Delay 4: NAND, NOT, NOR


Delay 10: AND, OR, XOR

CIS 351 Sample CL5 Problem Solutions

Thu 24th Sept, 2026

CL5: Propagation Delay

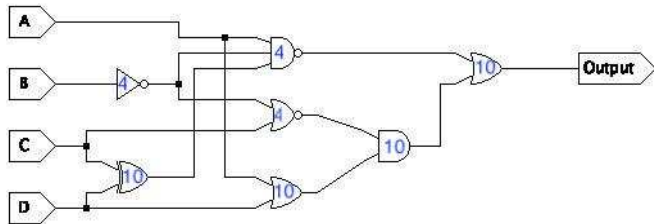Compute the propagation delay of the circuit below given the individual gate delays:



30

Circuit: $\overline{AB(C \oplus D)} + \overline{(\overline{B} + C)(A + D)}$

Delay 4: NAND, NOT, NOR

Delay 10: AND, OR, XOR